

Lab Report: 3

Name: Saarthak Sabharwal

Roll number: 2023102055

Group number: 6




Part-A

Objective: Designing 4:1 Multiplexer using basic logic gates

Electronic components used:


- Digital test kit (w/ breadboard)
- 1x 74HC04 IC
- 2x 74HC11 ICs
- 1x 74HC32 IC
- Wires

The reference circuit:

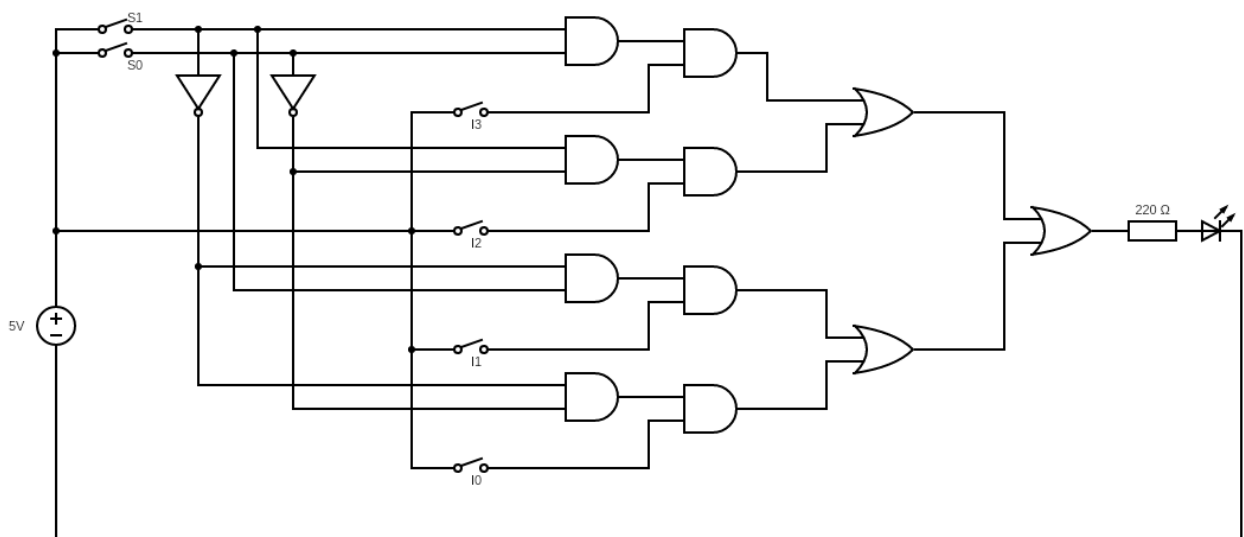

Procedure:

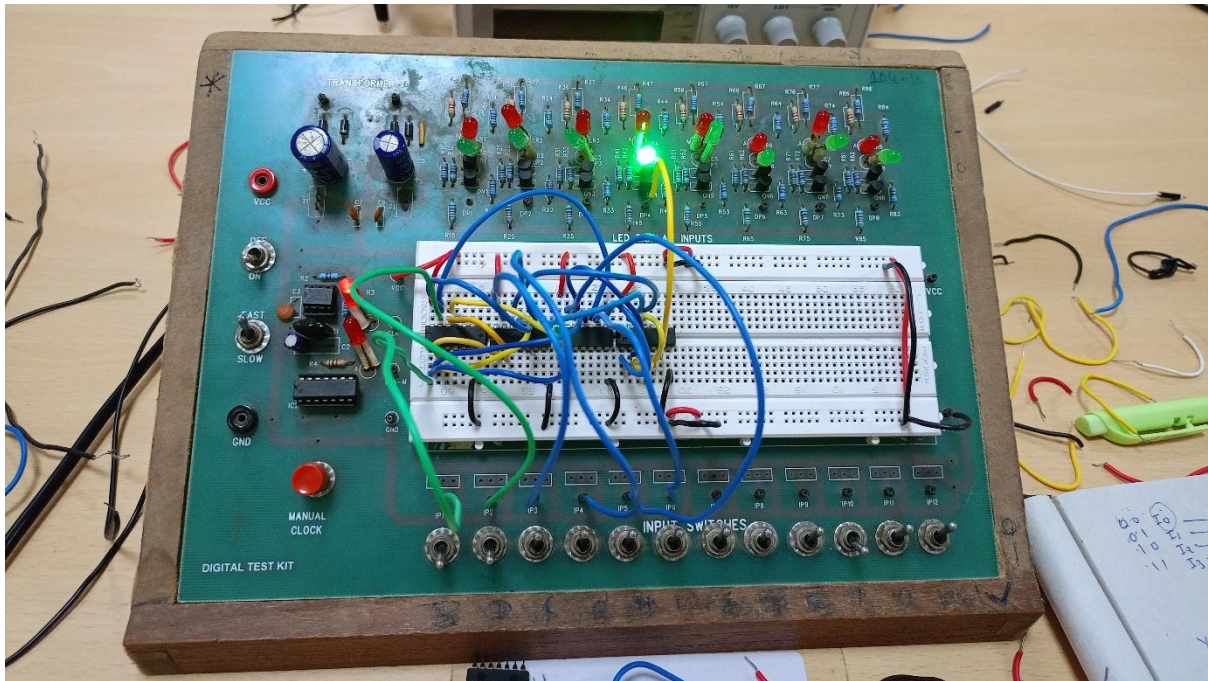- Set up the circuit on the breadboard as shown in the reference diagram.
- Observe outputs on the LED against all possible inputs through the toggles.
- Tabulate the observations into a truth table.



Conclusion: The truth table of a 4-to-1 multiplexer came out as:

S1	S0	Y
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃

Link for the Tinkercad simulation:

https://www.tinkercad.com/things/fldQ2UMQflx-l3parta/editel?sharecode=LDQL6a472cgXzCia6OoH2pR0e6nXj5h6j65p_Yz2s9Y


Part-B

Objective: Designing 1:4 Demultiplexer using basic logic gates

Electronic components used:


- Digital Test Kit (w/ breadboard)
- 1x 74HC04 IC
- 2x 74HC11 ICs
- Wires

The reference circuit:

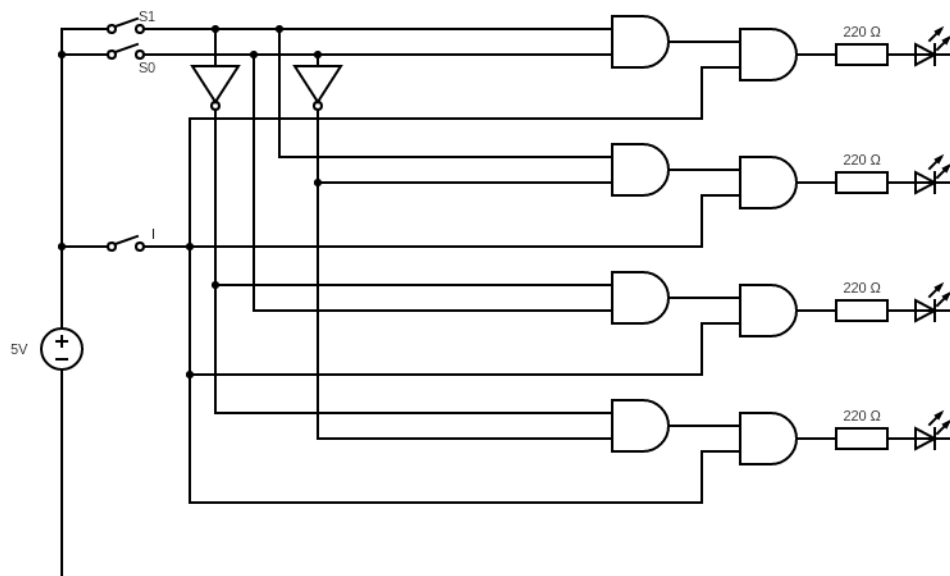

Procedure:

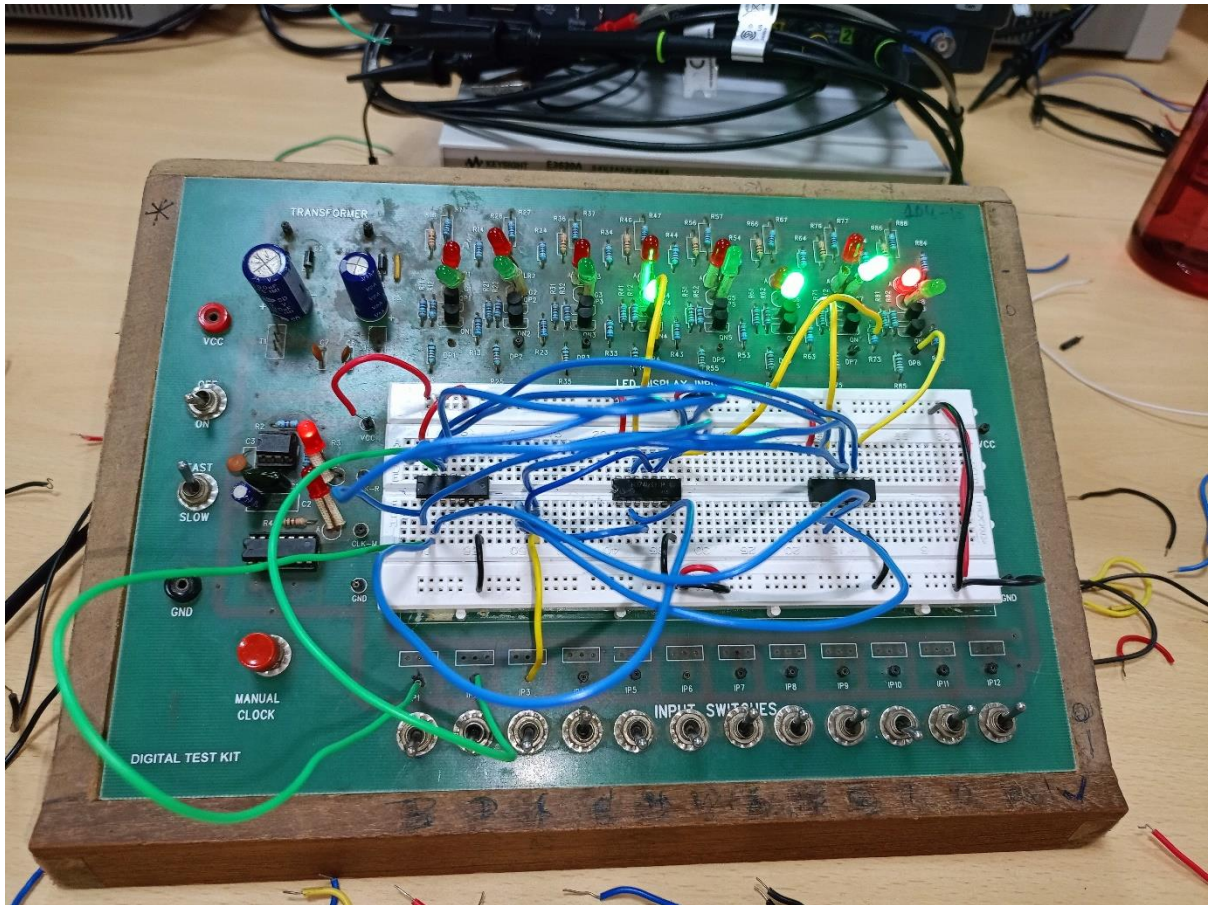- Set up the circuit on the breadboard as shown in the reference diagram.
- Observe outputs on the LEDs against all possible inputs through the toggles.
- Tabulate the observations into a truth table.



Conclusion: The truth table of a 4-to-1 multiplexer came out as:

S1	S0	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Link for the Tinkercad simulation:

https://www.tinkercad.com/things/3RcMGpTZToM-l3partb/editel?sharecode=M_ennQyRwCt35bX9hbljiU04xZV4-pmhyoohJZpRCyg


Part-C

Objective: Assembling the Mux-Demux circuit and testing it with Arduino

Electronic components used:

- Digital test kit (w/ breadboard)
- Part-A circuit
- Part-B circuit
- Arduino Uno
- Wires

The reference circuit:


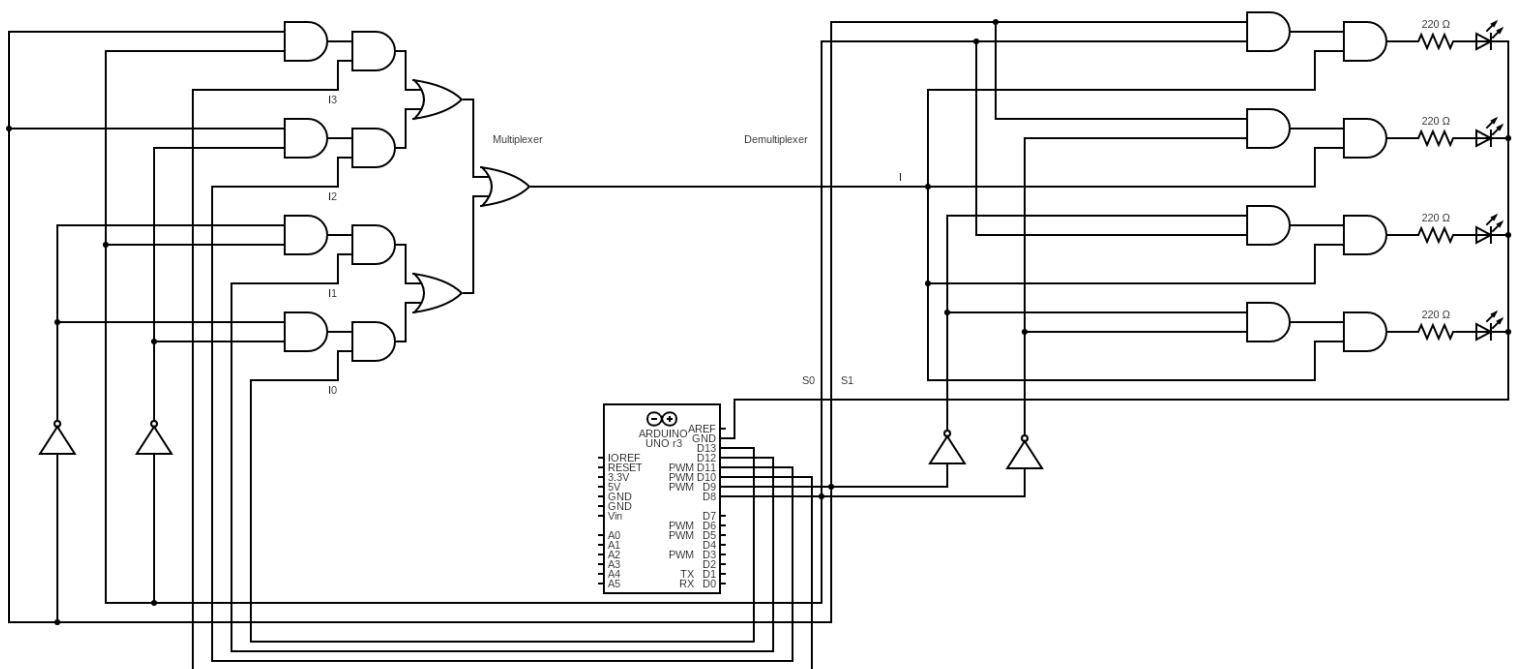


Arduino Code:

```
1 //Auth: @Saarthak_2023102055
2 //Mux-Demux Controller
3 //Accepts serial input in the format:
4 // S0|S1|I0|I1|I2|I3 0|1
5 //to set the values for Select/Input switches
6
7 int S[] = {9, 8};
8 int I[] = {13, 12, 11, 10};
9 void setup()
10 {
11     Serial.begin(9600);
12     for(int i = 8; i <= 13; i++)
13         pinMode(i, OUTPUT);
14 }
15
16 void loop()
17 {
18     while(!Serial.available());
19
20     String cmd = Serial.readString();
21     Serial.println(cmd);
22
23     switch(cmd[0]) {
24         case 'S':
25             digitalWrite(S[cmd[1]-'0'], cmd[3]-'0');
26             break;
27         case 'I':
28             digitalWrite(I[cmd[1]-'0'], cmd[3]-'0');
29             break;
30     }
31 }
```

Procedure:

- Connect the final output of the multiplexer to the input of the demultiplexer instead of the LED.
- Replace the data inputs to the multiplexer with pins 13, 12, 11 and 10.
- Replace the select inputs to both the circuits with pins 9 and 8.
- Remove the power supply and ground the common cathode of the demultiplexer output LEDs using the GND pin.
- Compile and upload the program shown to Arduino.
- Provide inputs through the pins using the Serial Monitor.

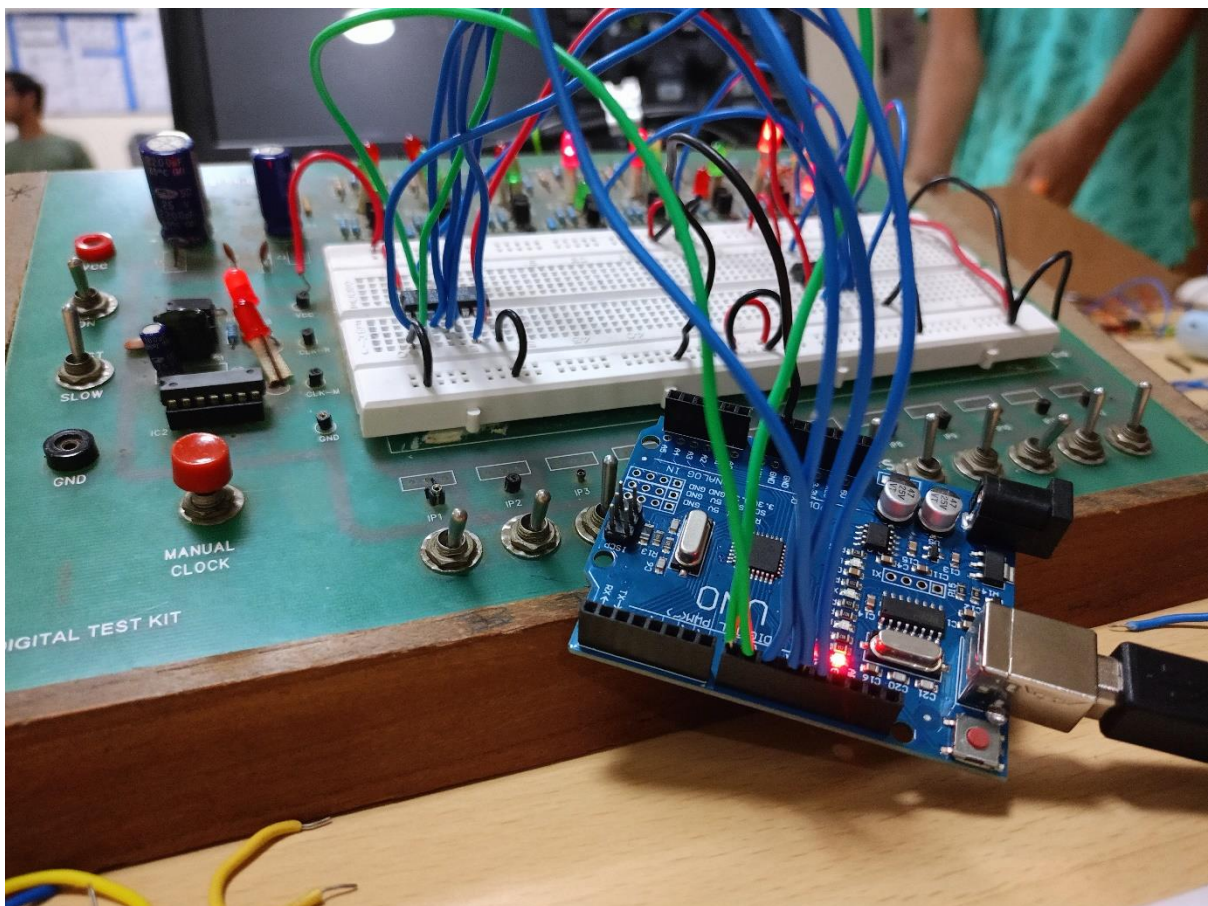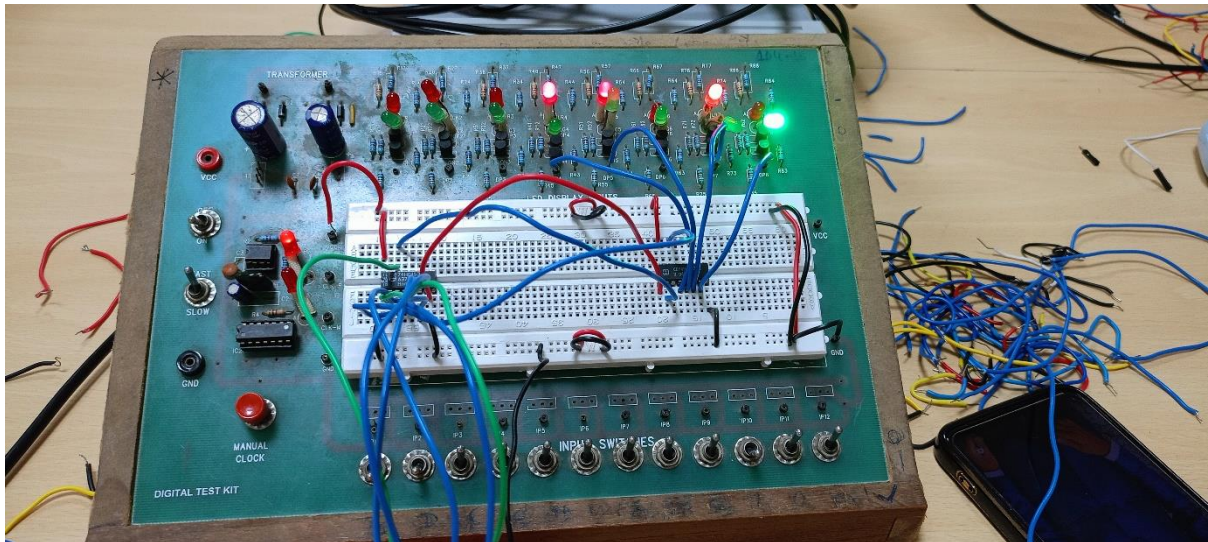

Conclusion: The assembled Mux-Demux circuit came out to be functional and consistent.

Link for the Tinkercad simulation:

<https://www.tinkercad.com/things/3wIBNjSlx9-l3partc/editel?sharecode=wI2vTp3qOTJA79cqttY1ZsQxW2ST3D5nbn3KhC5nW7Y>